



# Register

# Chapter-1

## Transfer and Micro-operations


---

- 1.1 Register – Transfer Language
- 1.2 Register Transfer
- 1.3 Bus Transfer and Memory Transfer
- 1.4 Arithmetic Micro-Operations
- 1.5 Logic micro operations Shift Micro
- 1.6 operation. Arithmetic Logic Shift
- 1.7 Unit



# Micro-operations

Ref. Book Name : Computer System Architecture, M. Morris Mano

- ❑ Micro-operations are elementary operations performed on data store in registers or in memory.
  
  - ❑ The Micro-operations most frequently encountered are of four types:
    - i. Transfer Micro-operations
    - ii. Arithmetic Micro-operations
    - iii. Logic Micro-operations
    - iv. Shift Micro-operations
- 

# 1.1 Register Transfer Language

Ref. Book Name : Computer System Architecture, M. Morris Mano

- ❑ The symbolic notation used to describe the micro-operation transfers among registers is called a register transfer language.
- ❑ Information transferred from one register to another is designated by means of a replacement operator.
- ❑ The statement Denotes a transfer of the content of register R1 into register R2.

$$R2 \leftarrow R1$$


- ❑ The content of source register R1 does not change after the transfer.

## 1.2 Register Transfer

- When data is transferred from one register to another register is known as register transfer.
- Computer registers are designated by capital letters to denote the function of the register.




(a) Register

 

(b) Showing individual bits



(c) Numbering of bits

 

(d) Divided into parts



## 1.2 Register Transfer

- ▣ To denote a transfer to occur only under a predetermined control condition

if (P=1) then (R2  $\leftarrow$  R1)

- ▣ Where P is a control signal generated in the control section.
- ▣ The control function is a Boolean variable that is equal to 1 or 0. It can also be denoted by

P : R2  $\leftarrow$  R1

- ▣ Control condition symbolizes the requirement that the transfer operation be executed by the hardware only if P=1.

# Transfer between registers


 


Figure: Transfer from R1 to R2, when P=1.

 

Timing diagram



## 1.3 Bus and Memory Transfers

- ❑ Transferring information between registers in a multiple register configuration is a common bus system.
- ❑ A bus structure consists of a set of common lines through which binary information is transferred one at a time.
- ❑ Control signals determine which register is selected by the bus during each particular register transfer.
- ❑ One way of constructing a common bus system is with multiplexers.
- ❑ The multiplexers select the source register whose binary information is then placed on the bus.
- ❑ The selection lines (S1, S0) choose the four bits of the register and transfer them to four line common bus.


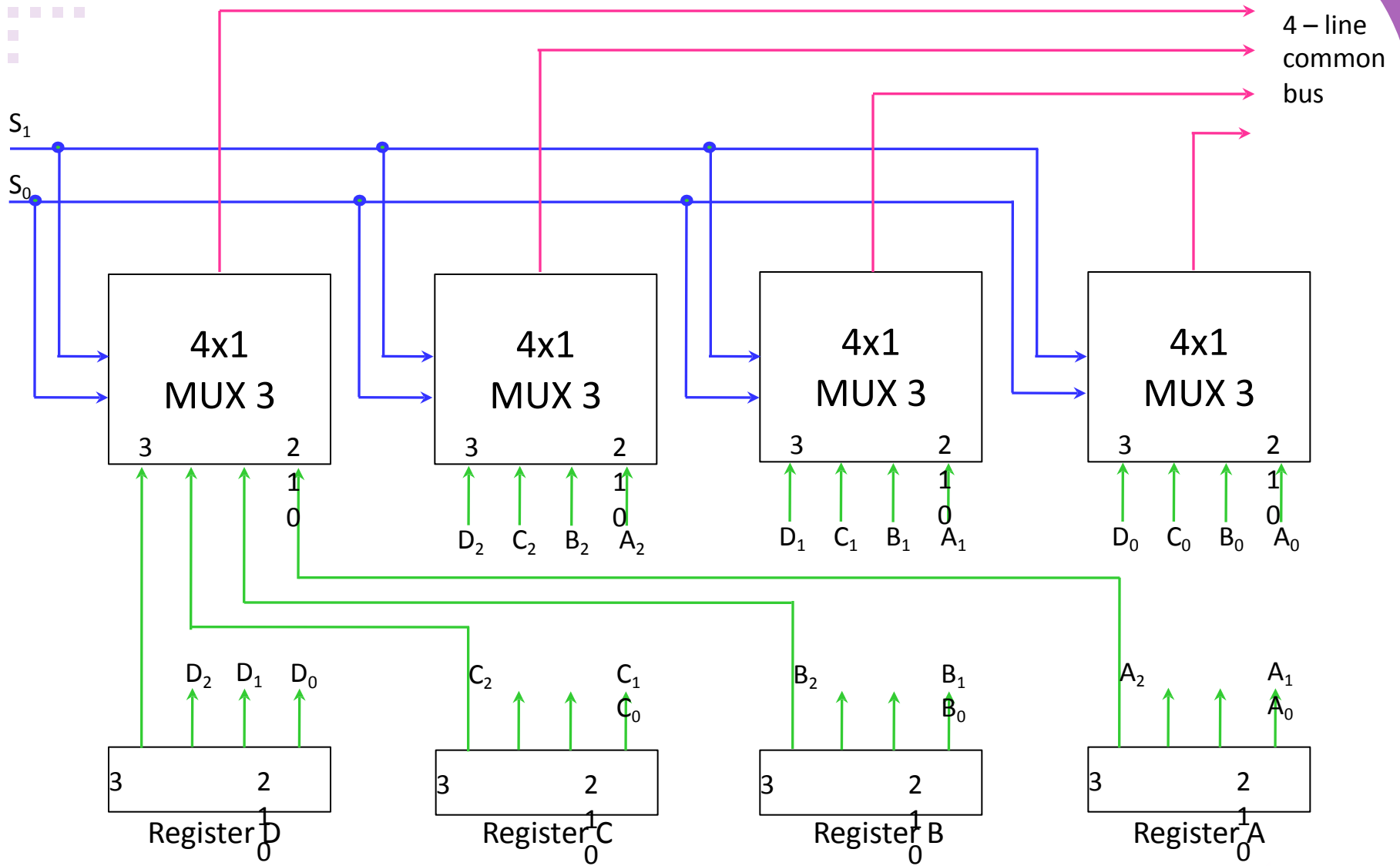


Figure: Bus system for four registers

 

# Three state Bus Buffers

- ❑ Buffer is a circuit used to boost up the signals for transmitting over long distance.
- ❑ Three state gate is a digital circuit that exhibits three states.
- ❑ Two of the states are signals equivalent to logic 1 and 0.
- ❑ The third state is a high-impedance state.



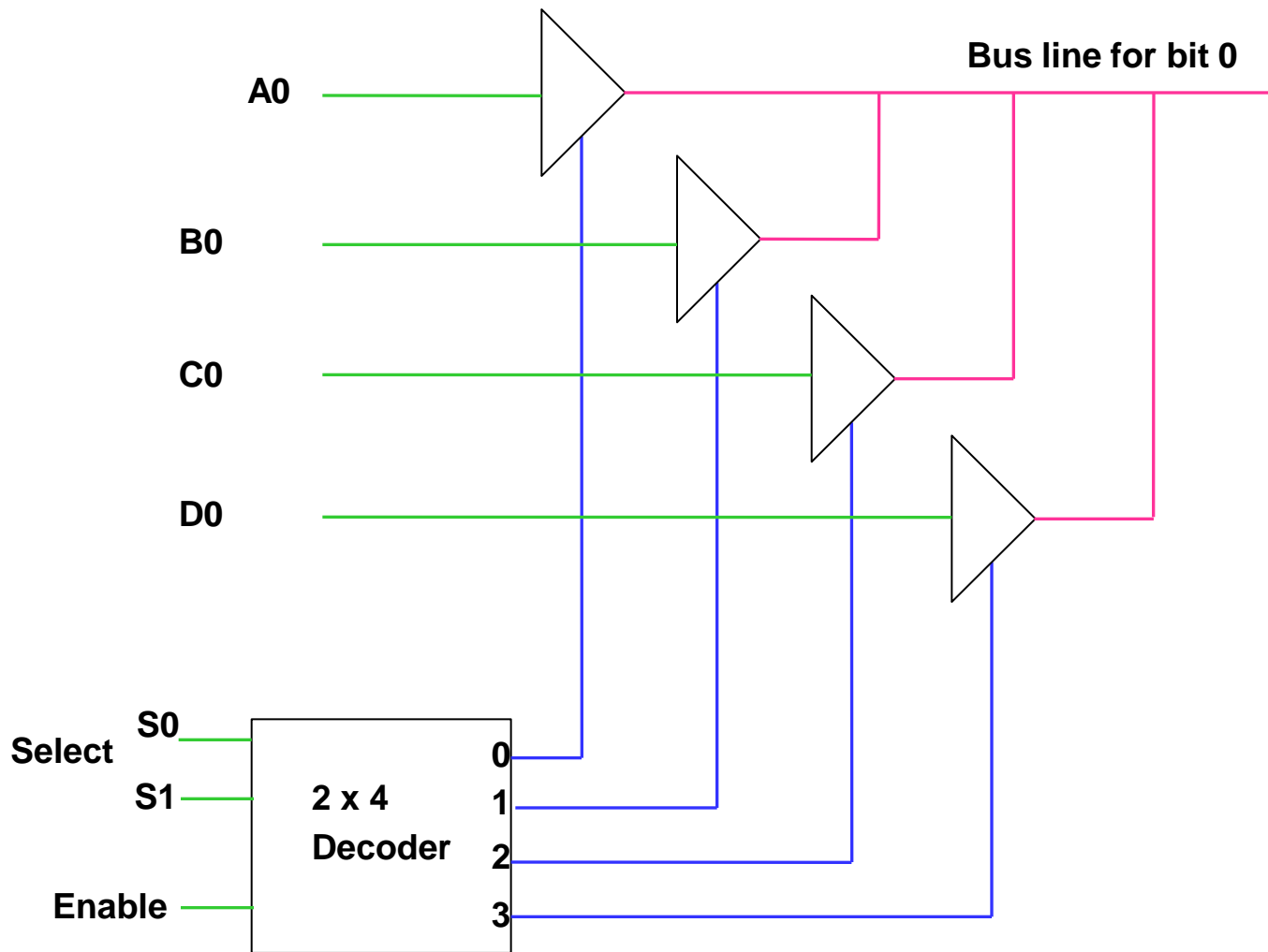



Figure: Bus Line with three state buffer

# Memory Transfer

- ❑ The transfer of information from memory to external environment is called a read operation.
- ❑ Transfer of new information to be stored into memory is called a write operation.

❑ Read :  $DR \leftarrow M[AR]$

❑ Write :  $M[AR] \leftarrow R1$

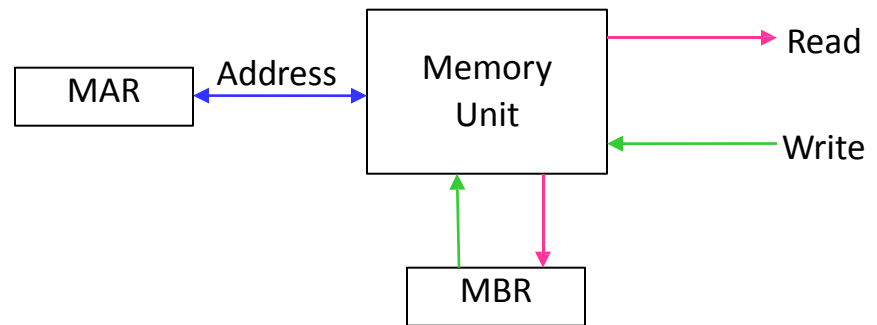

R :  $MBR \leftarrow MAR$

[MAR : Memory Buffer Register]

W :  $MAR \leftarrow MBR$

[MBR : Memory Address Register]

# 1.4 Arithmetic Micro operations

Ref. Book Name : Computer System Architecture, M. Morris Mano

Basic arithmetic micro operations are addition, subtraction, increment, decrement and shift.

$$R3 \leftarrow R1 + R2$$

$$R3 \leftarrow R1 - R2$$

$$R2 \leftarrow \overline{R2}$$

$$R2 \leftarrow \overline{R2} + 1$$

# Binary Adder

- Digital circuit that generates the arithmetic sum of two binary numbers of any length is called binary adder.

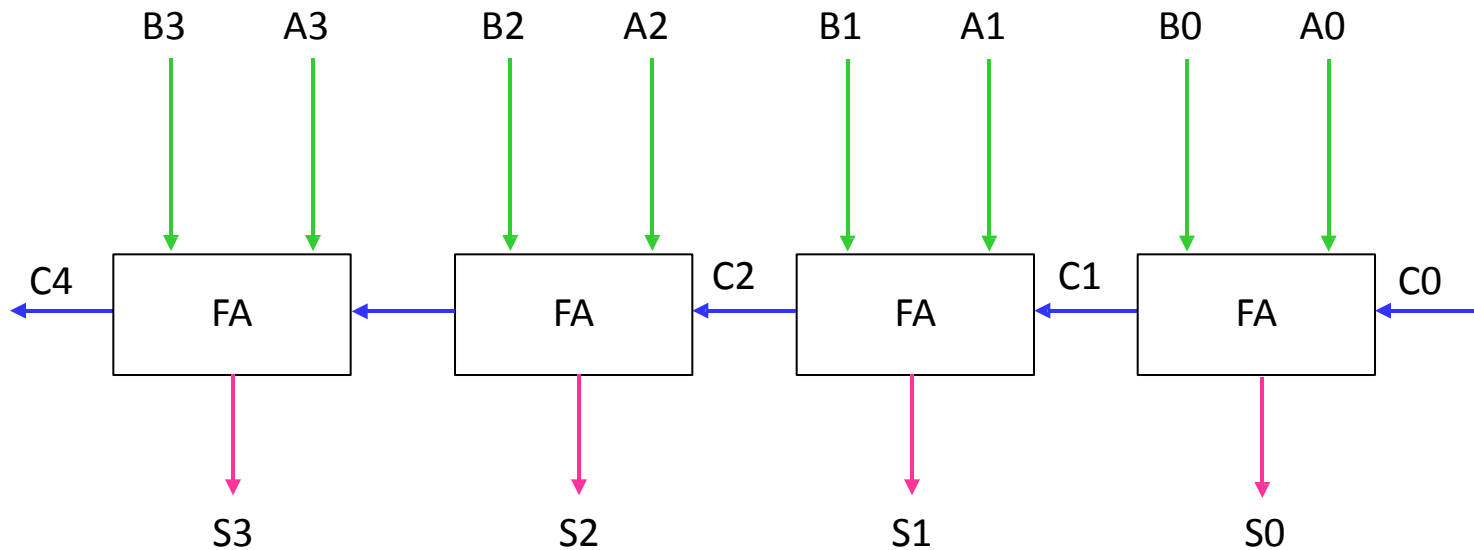


Figure: 4-bit binary adder

# Binary Adder-Subtractor

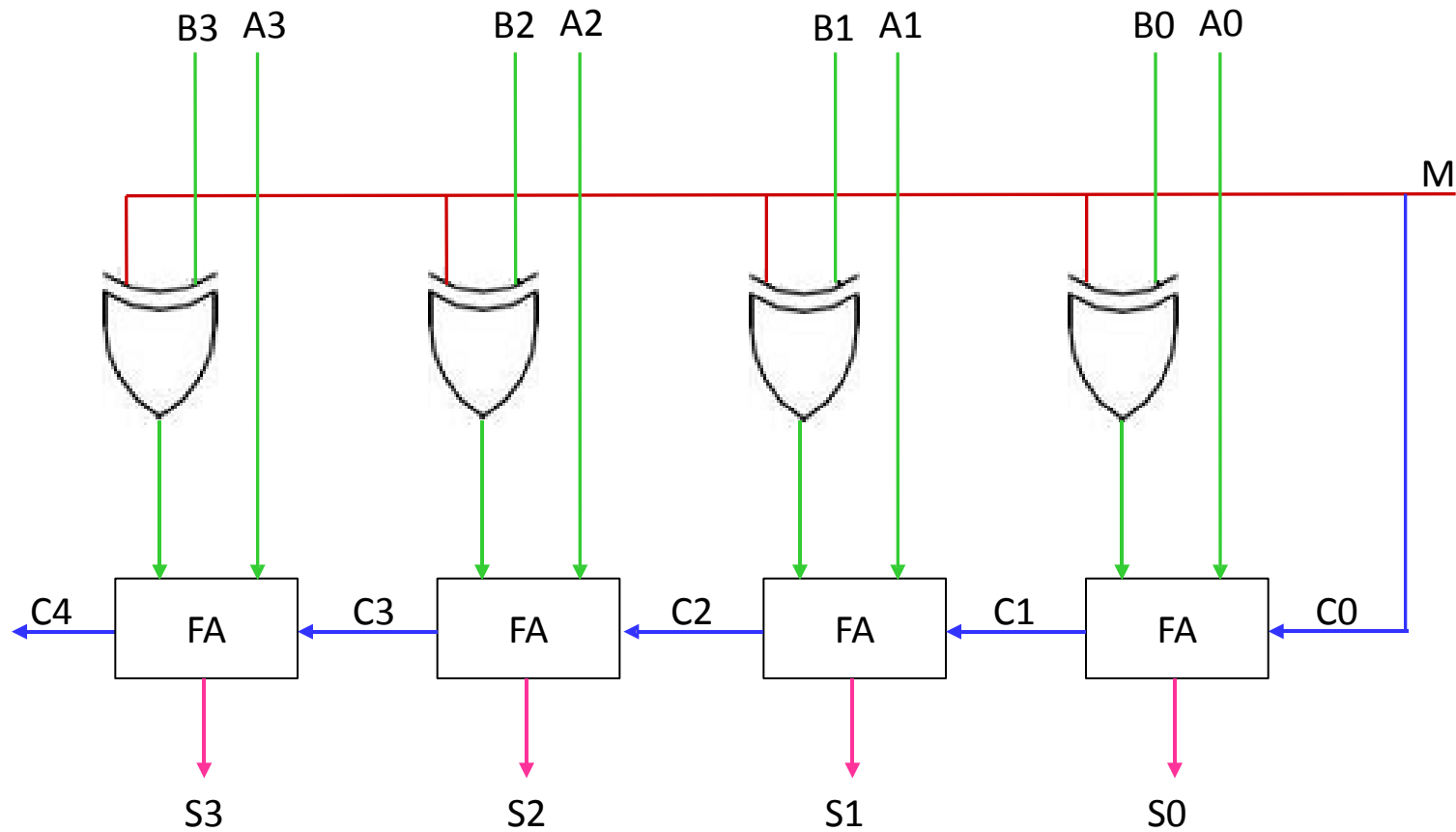


Figure: 4-bit binary adder-subtractor




# Binary Adder-Subtractor

- ❑ The subtraction  $A-B$  can be done by taking the 2's complement of  $B$  and adding it to  $A$ .
- ❑ The mode input  $M$  controls the operation.
- ❑ When  $M=0$  the circuit is an adder.
- ❑ When  $M=1$  the circuit becomes a subtractor.
- ❑ Each exclusive-OR gate receives input  $M$  and one of the inputs of  $B$ .
- ❑ When  $M=0$ , we have  $B \oplus 0 = B$ , Full adders receive the value of  $B$ , input carry is 0 ( $C_0$  is connected to  $M$ ), and circuit performs  $A+B$ .
- ❑ When  $M=1$ , we have  $B \oplus 1 = B'$  and  $C_0=1$ . The  $B$  inputs are all complemented ( $B'$ ) and 1 is added through input carry.
- ❑ Circuit performs  $A + 2$ 's complement of  $B$ .
 
# Binary Adder-Subtractor

- Subtraction of B from A is written as
- $A = A + 2\text{'s complement of } B \Rightarrow (B' + 1)$
- For example,  
 $A = 1011_2 = 11_{10}$   
 $B = 1001_2 = 9_{10}$
- 1's complement of register B is  $B' = 0110_2$
- 2's complement of B is  $B' + 1 = 0110 + 1 = 0111_2$
- Now add A to 2's complement of B





# Binary Incrementer

- The increment micro-operation adds one to a number in register.

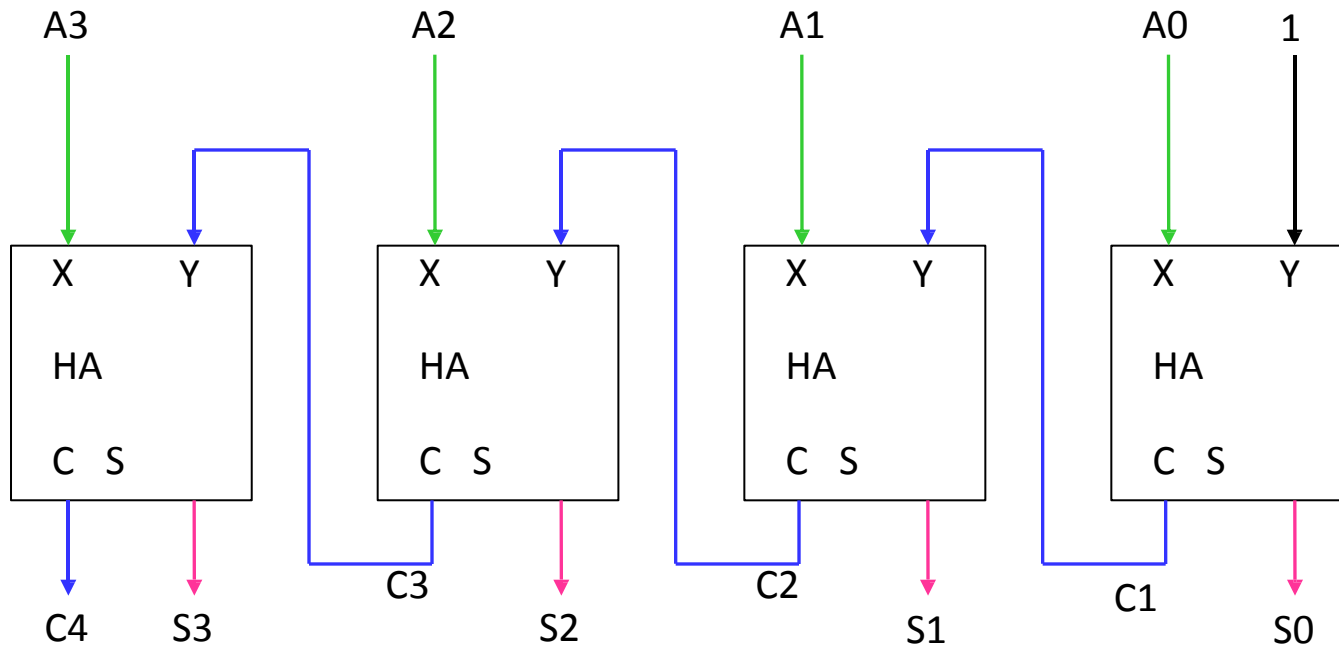


Figure: 4-bit binary incrementer



# Binary Incrementer

- ❑ One of the inputs of the half-adder is connected to logic 1.
- ❑ Other input is connected to the least significant bit of the number to be incremented.
- ❑ Output carry from one half-adder is connected to one of the inputs of the next higher order half-adder.
- ❑ Circuit receives four bits from A0 through A3, adds 1 to it, and generates the incremented output S0 through S3.
- ❑ Output carry C4 will be 1 only after incrementing binary 1111.
- ❑ Circuit can be extended to an n-bit binary incrementer by extending the diagram to include n half-adders.



# Arithmetic Circuit

- ❑ The basic component of an arithmetic circuit is the parallel adder.
- ❑ The four inputs from A go directly to the X inputs of the binary adder.
- ❑ Each of the four inputs from B are connected to the data inputs of the multiplexers.
- ❑ The data input of multiplexers also receive complement of B.
- ❑ The other two data inputs are connected to logic-0 and 1.
- ❑ The four multiplexers are controlled by two selection inputs, S1 and S0.
- ❑ The output of the binary adder is calculated from the following arithmetic sum:

$$D = A + Y + C_{in}$$

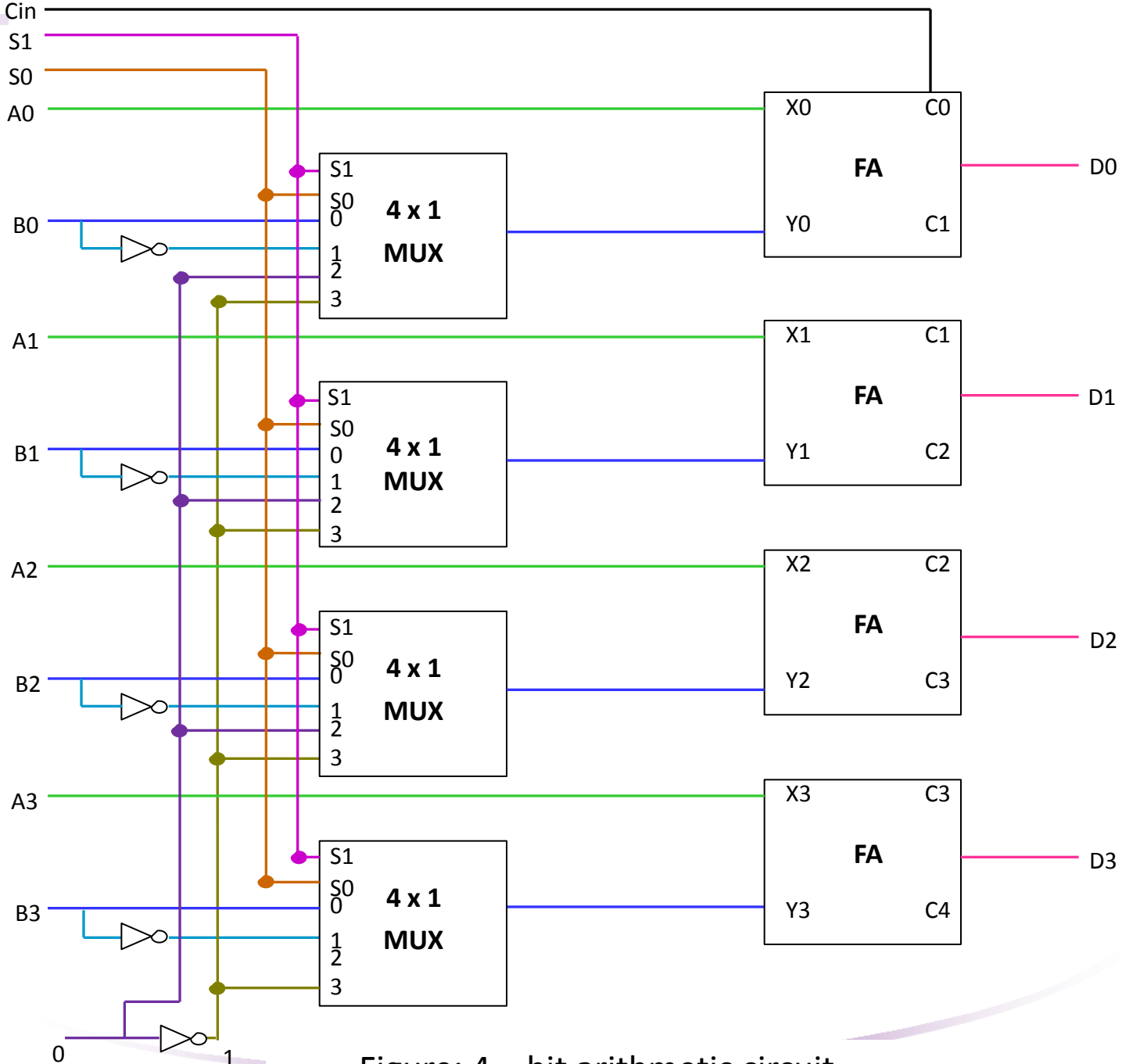


Figure: 4 – bit arithmetic circuit

# Arithmetic circuit function table

Select			Input	Output	Micro-operation
S1	S0	Cin	Y	$D=A+Y+Cin$	
0	0	0	B	$D=A+B$	Add
0	0	1	B	$D=A+B+1$	Add with carry
0	1	0	$B'$	$D=A+B'$	Subtract with borrow
0	1	1	$B'$	$D=A+B'+1$	Subtract
1	0	0	0	$D=A$	Transfer A
1	0	1	0	$D=A+1$	Increment A
1	1	0	1	$D=A-1$	Decrement A
1	1	1	1	$D=A$	Transfer A

# 1.5 Logic Micro-operations

Ref. Book Name : Computer System Architecture, M. Morris Mano

X Y	0	0	1	1	Boolean Function	Micro-operation	Name
	0	1	0	1			
	0	0	0	0	$F_0 = 0$	$F \leftarrow 0$	Clear
	0	0	0	1	$F_1 = XY$	$F \leftarrow A \wedge B$	AND
	0	0	1	0	$F_2 = XY'$	$F \leftarrow \overline{A} \wedge B$	
	0	0	1	1	$F_3 = X$	$F \leftarrow A$	Transfer A
	0	1	0	0	$F_4 = X'Y$	$\overline{F} \leftarrow A \wedge B$	
	0	1	0	1	$F_5 = Y$	$F \leftarrow B$	Transfer B
	0	1	1	0	$F_6 \oplus Y$	$F \oplus A \quad B$	Exclusive OR
	0	1	1	1	$F_7 = X + Y$	$F \leftarrow A \vee B$	OR

# 1.5 Logic Micro-operations

X Y	0	0	1	1	Boolean Function	Micro-operation	Name
	0	1	0	1			
	1	0	0	0	$F_8 = (X + Y)'$	$F \leftarrow \overline{A \vee B}$	NOR
	1	0	0	1	$F_9 = (X \oplus Y)'$	$F \leftarrow \overline{A \oplus B}$	Exclusive NOR
	1	0	1	0	$F_{10} = Y'$	$\overline{F} \leftarrow B$	Complement B
	1	0	1	1	$F_{11} = X + Y'$	$F \leftarrow A \vee \overline{B}$	
	1	1	0	0	$F_{12} = X'$	$\overline{F} \leftarrow A$	Complement A
	1	1	0	1	$F_{13} = X' + Y$	$F \leftarrow \overline{A} \vee B$	
	1	1	1	0	$F_{14} = (XY)'$	$F \leftarrow \overline{A \wedge B}$	NAND
	1	1	1	1	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	Set to all 1's

# Hardware Implementation

- ❏ Logic micro-operations specify binary operations for strings of bits stored in register.
- ❏ Most computers use only 4 micro-operations :
  1. AND
  2. OR
  3. XOR
  4. Complement

S1	S0	Output	Operation
0	0	$E = A \wedge B$	AND
0	1	$E = A \vee B$	OR
1	0	$E = A \oplus B$	XOR
1	1	$E = \overline{A}$	Complement

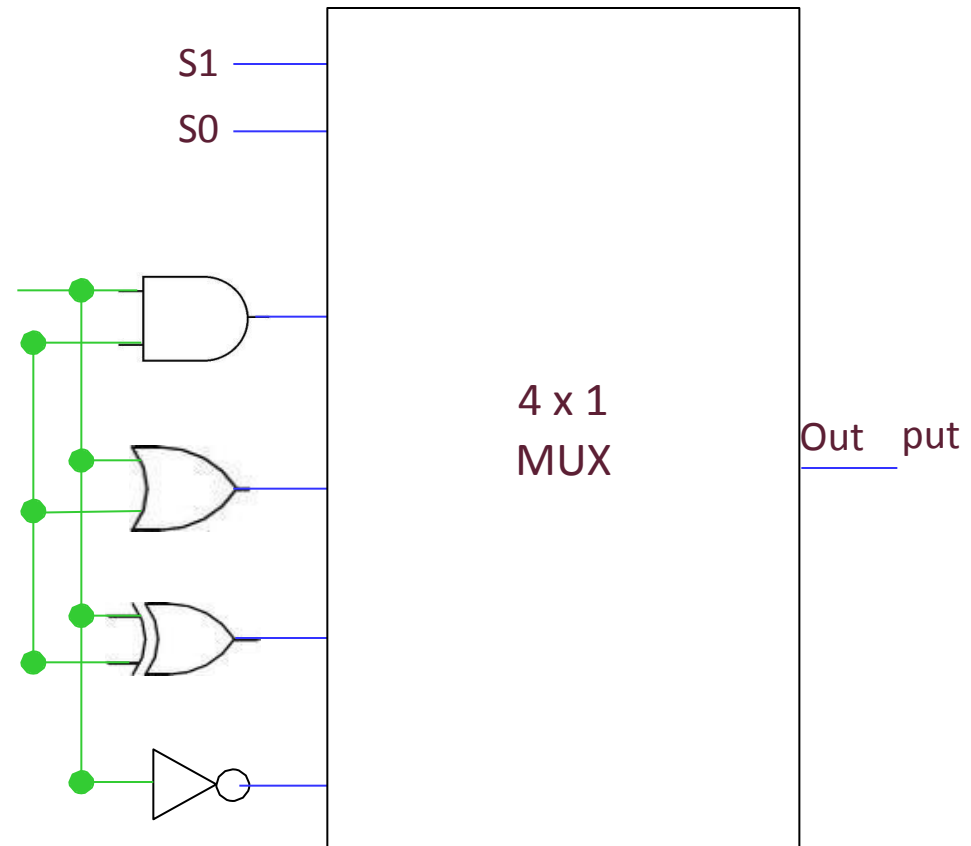


Figure: One stage of logic circuit



# Applications of Logic Micro-operation

## Selective set

- The selective set operation sets to 1 the bits in register A where there are corresponding 1's in register B.
- It does not affect bit positions that have 0's in B.
- For example:

$$\begin{array}{r} 1010 \quad \text{A before} \\ 1100 \quad \text{B logic operand} \\ \hline 1110 \quad \text{A after} \end{array}$$

- A: Processor Register
- B: Logic operand extracted from memory
- OR micro-operation can be used to selectively set bits of a register.

## Selective Complement

- This operation complements bits in A where there are corresponding bits in A where there are corresponding 1's in B.
- For example,

$$\begin{array}{r} 1\ 0\ 1\ 0 \\ \underline{\quad\quad\quad 1} \\ 0\ 1\ 0\ 0 \end{array}$$

A before  
B logic operand  
A after

- Exclusive-OR micro-operation can be used for selective complement.

## Selective Clear

- The selective clear operation clears to 0 the bits in A only where there are corresponding 1's in B.
- For example,

$$\begin{array}{r} 1\ 0\ 1\ 0 \\ \underline{\quad\quad\quad 1} \\ 0\ 1\ 0\ 0 \end{array}$$

A before  
B logic operand  
A after

- Corresponding logic micro-operation is  $A \leftarrow A \wedge B$



## Mask (Delete)

- The mask operation is similar to the selective clear operation except that the bits of A are cleared only where there are corresponding 0's in B.
- For example,

1 0 1 0	A before
1 1 0 0	B logic operand
<hr/>	
1 0 0 0	A after

- The mask operation is an AND micro-operation



## Insert

- The insert operation inserts a new value into group of bits.
- This is done by first masking the bits and then ORing them with the required value.
- For example,

$$\begin{array}{r} 01101010 \\ 00001111 \\ \hline 00001010 \end{array}$$

A before  
B (mask)  
A after masking

- Now insert the new value

$$\begin{array}{r} 01101010 \\ 10011111 \\ \hline 10011010 \end{array}$$

A before  
B (insert)  
A after insertion

# 1.6 Shift Micro-operations

Ref. Book Name : Computer System Architecture, M. Morris Mano

- ▣ Shift micro-operations are used for serial transfer of data.
- ▣ The contents of a register can be shifted to the left or to the right.
- ▣ The information transferred through the serial input determines the type of shift. There are three types of shifts:
  1. Logical Shift
  2. Circular Shift
  3. Arithmetic Shift



# 1.6 Shift Micro-operations

## 1. Logical Shift

- ❑ A logical shift is one that transfers 0 through the serial input.
- ❑ The symbols `shl` and `shr` denotes logical shift.

$R1 \leftarrow \text{shl } R1$

$R2 \leftarrow \text{shr } R2.$


## 2. Circular Shift (rotate operation)

- ❑ The circular shift circulates the bits of the register around the two ends without loss of information.
- ❑ `cil` denotes circular shift left
- ❑ `cir` denotes circular shift right.

# 1.6 Shift Micro-operations
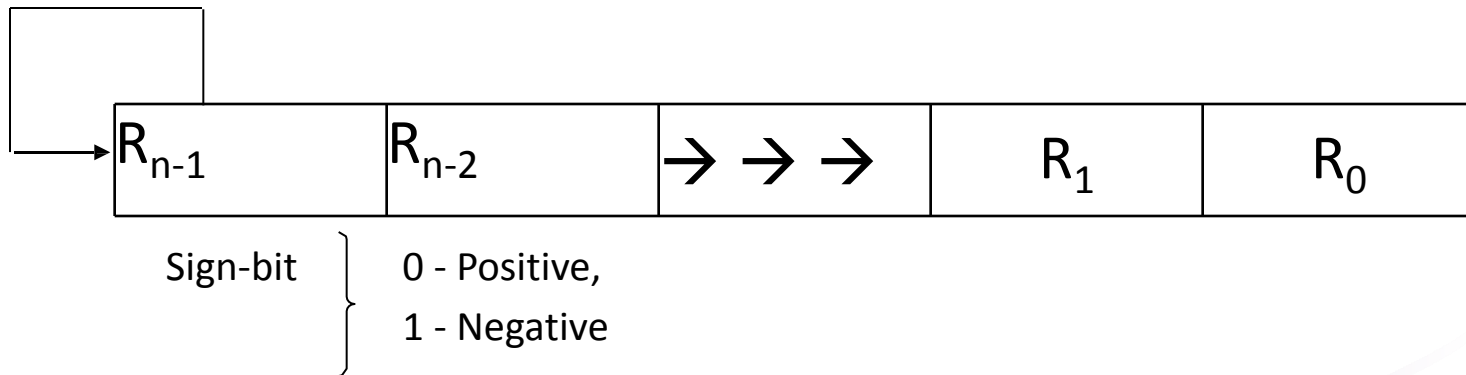
## 3. Arithmetic Shift

- ▣ An arithmetic shift is a micro-operation that shifts a signed binary number to the left or right.
- ▣ An arithmetic shift-left multiplies a signed binary number by 2.
- ▣ An arithmetic shift-right divides the number by 2.



# 1.7 Arithmetic Logic Shift Unit

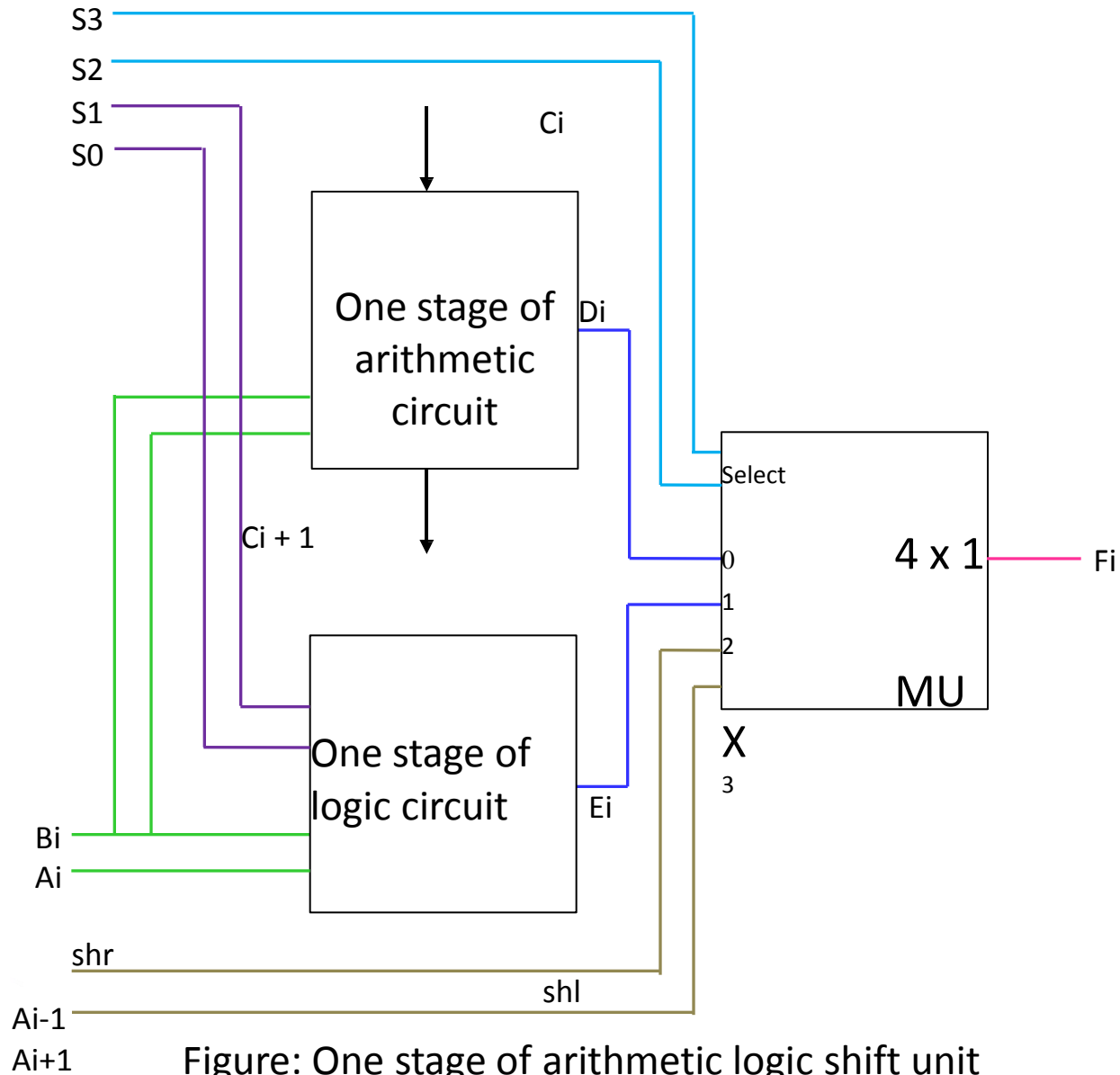


Figure: One stage of arithmetic logic shift unit



# Function table for Arithmetic Logic Shift Unit

Operation Select				Cin	Operation	Function
S3	S2	S1	S0			
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + B'$	Subtract with borrow
0	0	1	0	1	$F = A + B' + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	X	$F = A \wedge B$	AND
0	1	0	1	X	$F = A \vee B$	OR
0	1	1	0	X	$F = A \oplus B$	XOR
0	1	1	1	X	$F = A'$	Complement
1	0	X	X	X	$F = \text{shr } A$	Shift right A into F
1	1	X	X	X	$F = \text{shl } A$	Shift left A into F